



BALUCHISTAN UNIVERSITY OF ENGINEERING AND TECHNOLOGY KHUZDAR

DEPARTMENT: EED EXAMINATION: Mid Term 2021

SUBJECT: Electrical Network Analysis CODE: EE-211

SEMESTER: B.E(3rd Semester) Max: Marks: 20

Time Allowed: 40 Minutes

Note: Attempt All questions

Q.NO	Sub Q	Description	Marking Scheme	CLO/PLO	Bloom
1		Define the term Impedance, Admittance, Active Power, Reactive Power and Power Triangle	10	CLO-1 PLO-2	C-3
2.		Calculate the Laplace Transform of the following functions. (i) $F(t) = e^{-3t}$ (ii) $f(t) = \sin 3t$	5	CLO-1 PLO-1	C-1
3.		Explain the Resonance Circuit and derive the Resonant Frequency	5	CLO-1 PLO-1	C-1

THE END



BALUCHISTAN UNIVERSITY OF ENGINEERING AND TECHNOLOGY KHUZDAR

DEPARTMENT: EED EXAMINATION: Final Term 2021

SUBJECT: Electrical Network Analysis CODE: EE- 211

SEMESTER: B.E(3rd Semester) Max: Marks: 50

Time Allowed: 2 hour : 20 minutes

Note: Attempt All questions

Q.NO	Description	Marking Scheme	CLO / PLO	Bloom
1.	Explain the difference between STAR and DELTA connections. Find the current and the voltages across each element in Figure 1. Express each quantity also in polar form.	10	CLO-2 PLO-2	C-3
2.	Calculate the Impedance, Admittance, Conductance, and Capacitive Susceptance of Figure 2.	10	CLO-2 PLO-2	C-3
3.	State and explain the Z-parameters with basic equations, also Find the Z-parameters of the circuit given in Figure 3	10	CLO-1 PLO-2	C-1
4.	State and explain the loop and Node analysis, also calculate the current through 20 ohm resistor using Nodal Analysis as shown in Figure 4.	10	CLO-1 PLO-2	C-1
5.	Explain brief description of Two port Network, Series and Parallel Resonance, Initial Conditions, Poles and Zeros, and Fourier Series	10	CLO-2 PLO-2	C-3

THE END

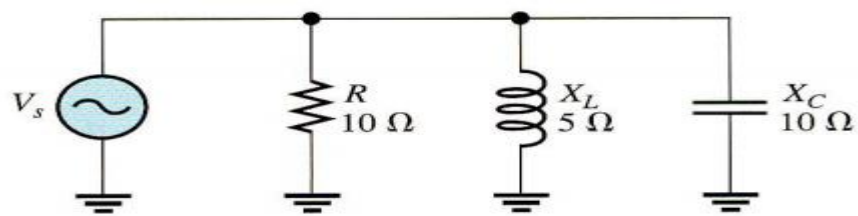


Figure 2

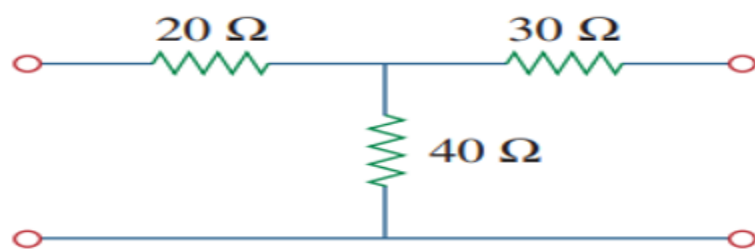


Figure 3

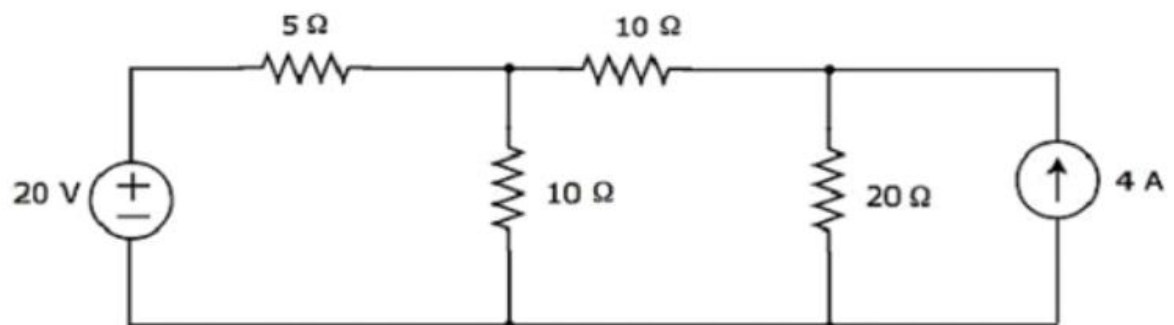


Figure 4